



K22U 1246

Reg. No. :

Name :

**II Semester B.C.A. Degree (C.B.C.S.S. – O.B.E. – Regular/Supplementary/
Improvement) Examination, April 2022
(2019 Admission Onwards)
Core Course
2B02BCA : DIGITAL SYSTEMS**

Time : 3 Hours

Max. Marks : 40

PART – A

Answer **all** questions. **Each** question carries **one** mark.

1. Give the base value and numbers of hexadecimal number system.
2. How many flip flops are needed for MOD 7 counter ?
3. In which input condition JK Flip Flop generates toggle output condition ?
4. Mention the number of input and output of demultiplexer.
5. List one example for sequential for a sequential circuit.
6. Specify any one error detection code.

PART – B

Answer **any six** out of eight. **Each** question carries **two** marks.

7. What is full adder ?
8. What is demultiplexer ?
9. What is latch ?
10. What are up/down counter ?
11. What is a register ?

P.T.O.



12. Why NAND is known as a universal gate ?
13. Define a Karnaugh map and state its use.
14. Draw the block diagram of clocked RS flip-flop.

PART – C

Answer **any four** out of six. **Each** question carries **three** marks.

15. What is a flip flop ?
16. Explain different types of shift registers.
17. State the laws and rules of Boolean algebra.
18. Show the steps in converting a binary number to its equivalent gray code .
19. Give the logic symbol of Master Slave J-K flip-flop.
20. Give the timing diagram for 3 bit synchronous counter.

PART – D

Answer **any two** out of four. **Each** question carries **five** marks.

21. Describe different types of gates with truth tables.
 22. Explain Demultiplexer with logic diagram.
 23. Write notes on full adder.
 24. Explain mod 10 Asynchronous counter.
-